



1 - Electricity Revision

1. A 200m sprinter records the following times over the course of a season:

19.83 s, 19.23 s, 19.56 s, 19.87 s, 19.40 s, 19.38 s, 19.73 s and 19.69 s.

Calculate or find:

a) Mean time of the sprinter. (1)

b) Random uncertainty in the mean. (3)

c) Mean Time \pm Random Uncertainty. (1)

2. The following readings were taken to measure the capacitance of a capacitor.

Charge, $Q = (10.8 \pm 0.01) \times 10^{-3} \text{C}$

Voltage, $V = (12.00 \pm 0.05) \text{V}$

Calculate or find:

a) Capacitance of the capacitor in micro Farads. (**$\times 10^{-6}$ Farads.**) (3)


b) Percentage uncertainty in the capacitance. (2)

c) Absolute uncertainty in the capacitance. (1)

d) Capacitance \pm Absolute Uncertainty. (1)

3. Calculate the resistance between points **G** and **H** in the circuit network below.

(3)

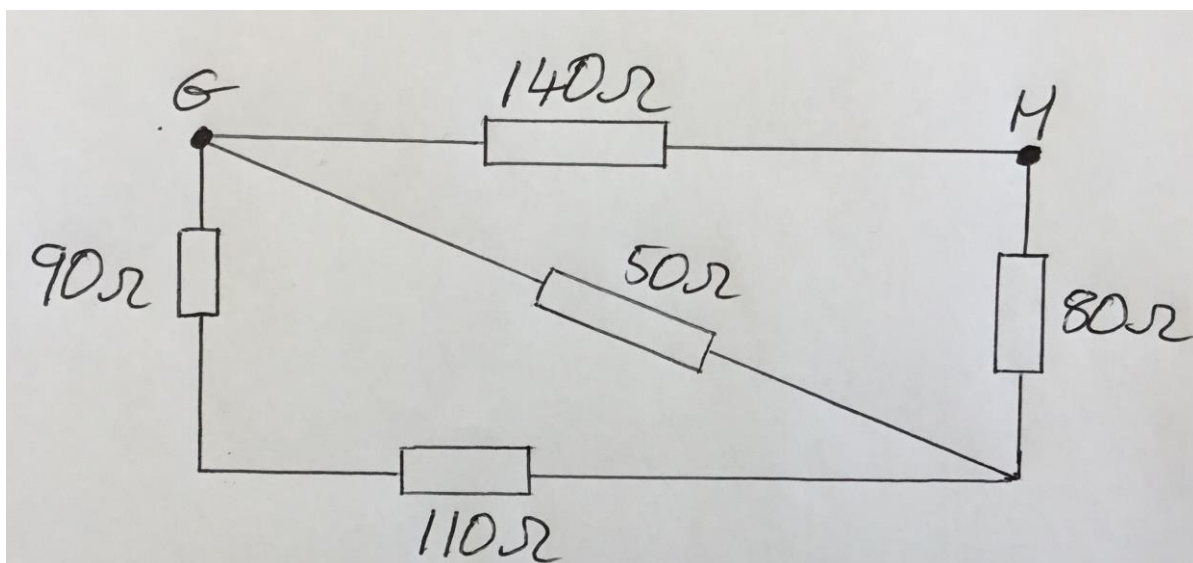


4. Calculate the readings on the **ammeter** and the **voltmeter** in the circuit below when:

a) The switch S is open.


(4)

b) The switch S is closed.

(4)

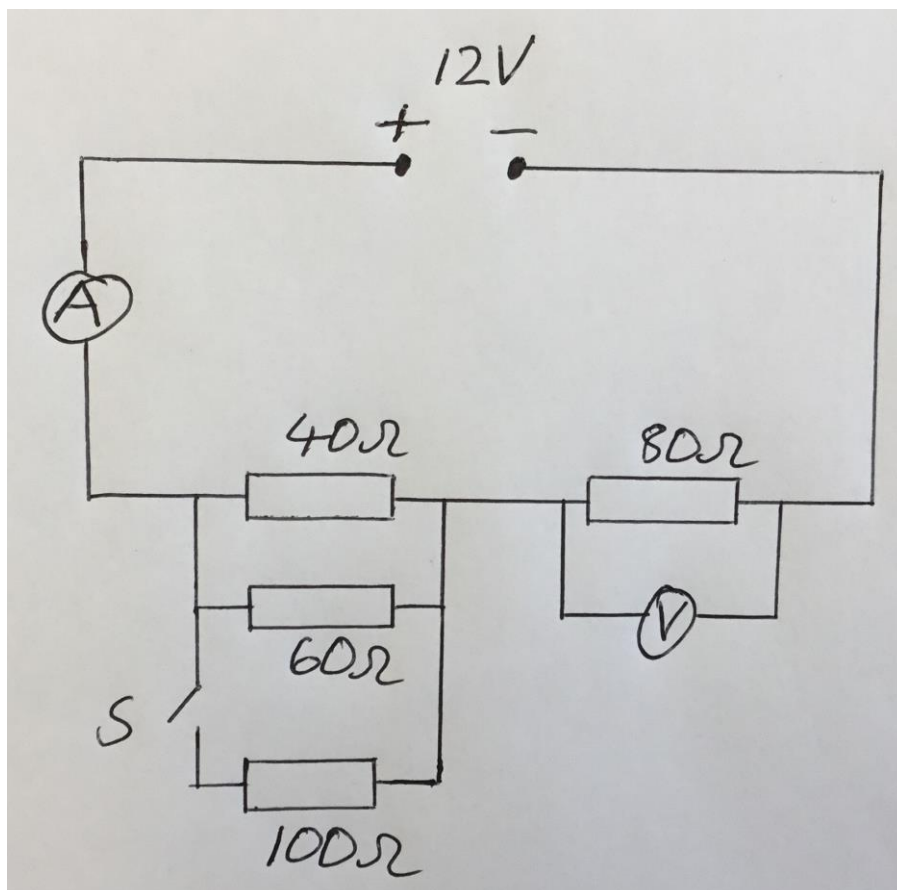

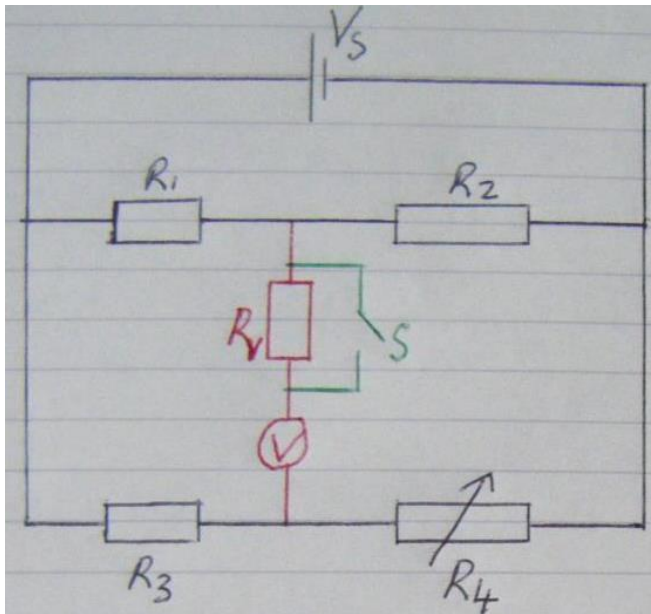5. The circuit diagram below shows a Wheatstone Bridge Circuit.



$$R_1 = 2.6 \text{ k}\Omega$$


$$R_2 = 4.2 \text{ k}\Omega$$

$$R_3 = 3.9 \text{ k}\Omega$$

$$R_4 = ?$$

- Calculate the resistance of variable resistor R_4 which will balance the Wheatstone Bridge. (3)
- What affect would an increase in the voltage supply from 8V to 12V have on the reading on the voltmeter when the bridge is balanced or when it is unbalanced? (2)
- What is the purpose of the switch S in this circuit? (1)

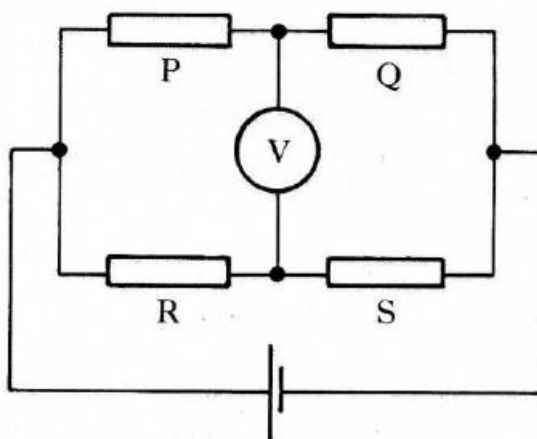6. Calculate the reading on the voltmeter in the unbalanced Wheatstone Bridge circuit below. (3)



$$P = 6.5 \text{ k}\Omega$$


$$Q = 3.5 \text{ k}\Omega$$

$$R = 2.1 \text{ k}\Omega$$

$$S = 8.2 \text{ k}\Omega$$

$$V_s = 10V$$

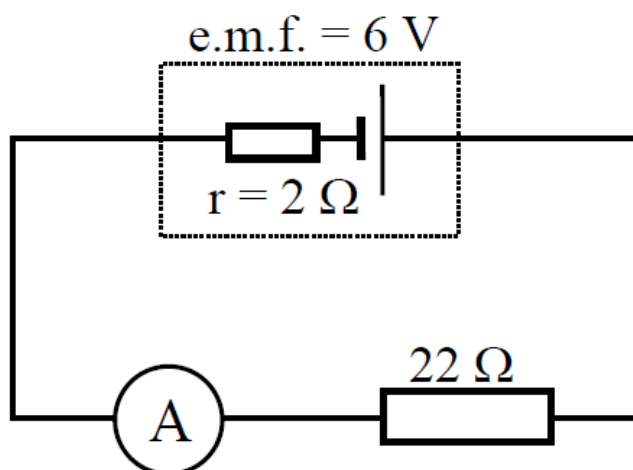7. Calculate or find the following from the circuit diagram below:



a) i) The current reading on the ammeter. (3)

ii) The terminal potential difference. (3)

iii) The lost volts. (1)

b) A voltmeter is placed across the cell and then a $66\ \Omega$ resistor is placed **in parallel** across the $22\ \Omega$ external load resistor.

Explain the changes observed on the readings found on the **ammeter** and the **voltmeter** when the $66\ \Omega$ resistor is added in parallel. (3)


8. A lamp is connected to an ac supply with the following readings being taken:

Peak Voltage = 325.3V

Peak Current = 369mA

Calculate the **power of the lamp**. (4)

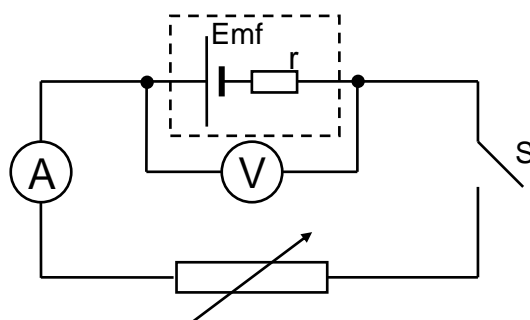9. A battery is connected in a circuit to look at how the voltage from a battery varies with the current drawn from it.



For each setting of the variable resistor the switch is closed for a short period of time, and the ammeter and voltmeter readings are recorded. A table of the results recorded is shown below.

Voltmeter reading (V)	5.5	4.5	3.5	2.5	1.5
Ammeter Reading (A)	5	15	25	35	45

- a) Draw a graph of the **voltmeter** reading **against** the **ammeter** reading using all the data from the table. (3)


- b) From the information in the graph find:
 - i) **e.m.f.** of the battery. (1)

 - ii) the **internal resistance** of the battery. (3)

 - iii) the **current** drawn from the battery if it is short circuited. (1)

- c) State the definition of e.m.f **using the figure found** in b) i). (1)

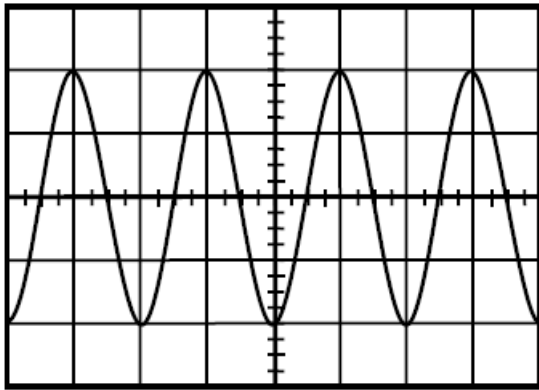10. A signal generator is connected to an oscilloscope and the trace below is observed on the oscilloscope screen.



Oscilloscope Settings

Y- Gain Setting = 10V div^{-1}

Time - Base Setting = 40ms div^{-1}


Calculate or find:

- a) Peak Voltage, V_p . (2)
- b) Root mean Square Voltage, V_{rms} . (2)
- c) Frequency, f . (4)

The time base setting is then reduced to 20ms div^{-1} .


- d) **Describe** the wave trace now observed on the screen. (2)

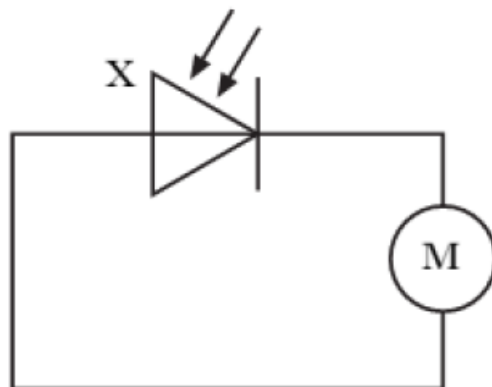11. In the diagram below the photodiode is used to turn the electric motor.



- a) In which mode is the photodiode operating? (1)
- b) Describe how the photodiode operates in this mode using the terms **junction, holes, electrons, photons and free charge carriers**. (3)

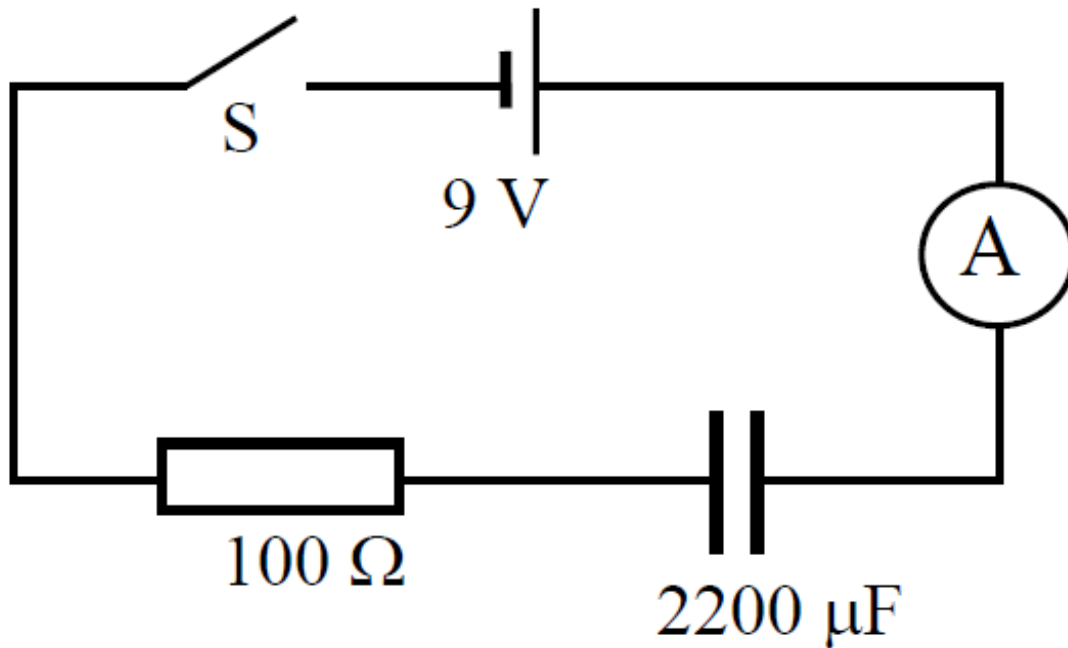
12. In the circuit below a potential divider is set up with a resistor, capacitor and a 9V battery.



The capacitor is initially uncharged.

- a) State the definition of a **2200μF** capacitance. (1)
- b) Calculate the reading on the ammeter at the instant that the switch S is closed. (3)
- c) State a suitable **range** for the ammeter. (1)
- d) Calculate the reading on the ammeter during the charging process when the voltage across the capacitor is 6V. (3)
- e) Calculate the charge stored in the capacitor when it is fully charged. (3)
- f) Calculate the energy stored in the capacitor when it is fully charged. (3)
- g) i) Sketch a graph of **current against time** during the charging of the capacitor. (Label the maximum current.) (2)
- ii) Sketch a graph of **voltage across the capacitor** against time during the charging of the capacitor. (Label the maximum voltage.) (2)

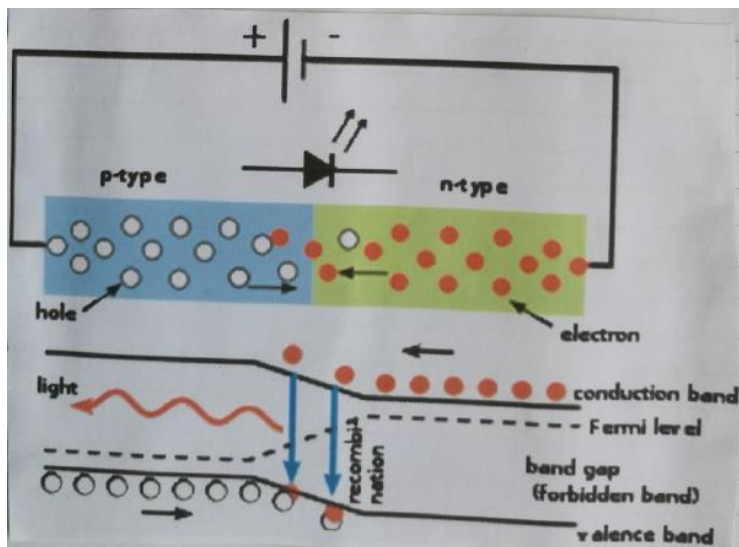13. a) Name the process which will convert a pure semiconductor material into a n-type semiconductor material. (1)
- b) Describe how this process will reduce the resistance of the semiconductor material. (2)
- c) State the name of the majority charge carriers in a n-type semiconductor material. (1)
14. a) **Draw band diagrams side by side** for insulators, semiconductors and conductors. (3)
- b) Describe the relative abundance of electrons contained in the bands for insulators, semiconductors and conductors. (3)
- c) Use the diagram shown below to describe how LED's work. (3)



Total Marks = 100